

Berwickshire High School

Physics Department

S3 Physics • Electricity 1: Circuits and Resistance

Practice Test

Name: _____ Date: _____

Answer all questions. 20 marks. 30 minutes.

You may use the resistor colour-band reference sheet and the N5 relationships sheet.

Score

Percentage

Grade

/20

%

Section A

Each question is worth 1 mark. Circle the letter of the correct answer.

1.

1

Four circuit symbols, W, X, Y and Z, are shown. Which row identifies the components represented by these symbols?




- A W ammeter, X lamp, Y resistor, Z fuse
- B W voltmeter, X lamp, Y fuse, Z resistor
- C W ammeter, X lamp, Y fuse, Z resistor
- D W voltmeter, X motor, Y resistor, Z fuse
- E W voltmeter, X lamp, Y resistor, Z fuse


2.

1

Two circuits are used to determine the resistance of resistor R, as shown. Which row in the table identifies meter P, meter Q and meter S?

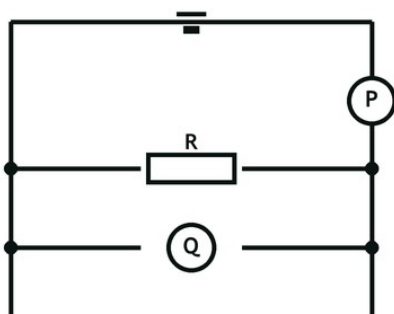

Circuit 1

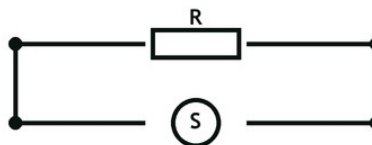

Circuit 2 – no supply


- A P voltmeter, Q ammeter, S ohmmeter
- B P ohmmeter, Q voltmeter, S ammeter
- C P ammeter, Q voltmeter, S ohmmeter
- D P ammeter, Q ohmmeter, S voltmeter
- E P voltmeter, Q ohmmeter, S ammeter

3.

1

The graph shows how the voltage varies with current for three resistors P, Q and R. A student makes the following statements. I The resistance of resistor P is greater than

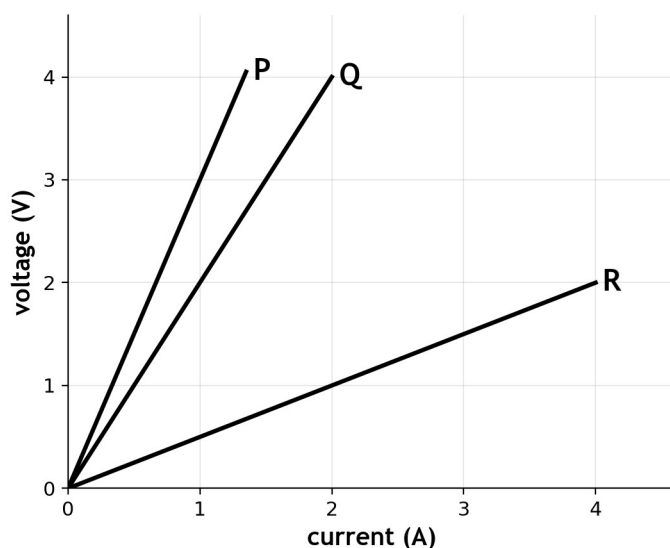that of resistors Q and R. II When the voltage across resistor Q is 2.0 V, the current in the resistor is 1.0 A. III The resistance of resistor R is $2.0\ \Omega$. Which of these statements is/are correct?



- A I only
- B II only
- C I and II only
- D II and III only
- E I, II and III

4.

1


The current in a circuit is a measure of the

- A energy given to each coulomb of charge
- B charge passing a point each second
- C speed of the charges in the wire
- D resistance of the circuit
- E voltage across the supply

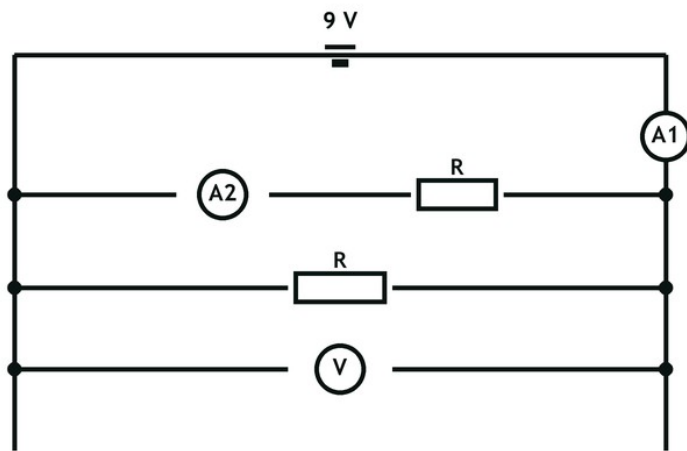5.

1

A circuit is set up as shown. The resistors are identical. Which row in the table shows the reading on the voltmeter and possible readings on ammeters A1 and A2?




- A 4.5 V, 0.4 A, 0.2 A
- B 9 V, 0.2 A, 0.4 A
- C 9 V, 0.4 A, 0.2 A
- D 4.5 V, 0.2 A, 0.2 A
- E 9 V, 0.2 A, 0.2 A

Section B

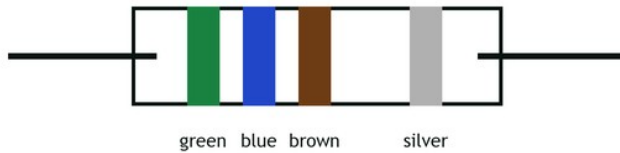6.


The diagram below shows the colour coding for a resistor. Using the information in the resistor colour-band reference sheet:



- (a) Determine the resistance of the resistor. 1
- (b) State the tolerance in the resistance of the resistor. 1
- (c) Determine the maximum value of resistance of the resistor. 1
- (d) Determine the minimum value of resistance of the resistor. 1

7.


A student sets up the circuit as shown.

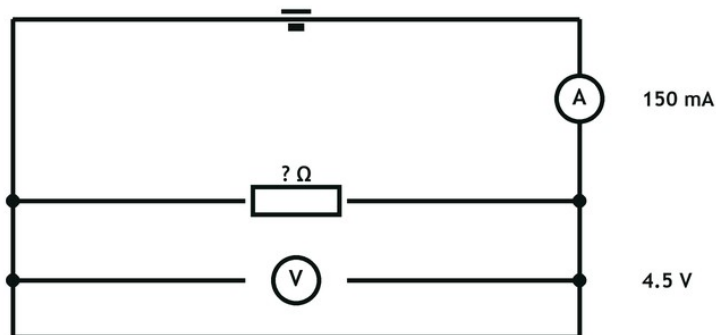

Calculate the resistance of the resistor. 3

8.

A circuit is set up as shown.

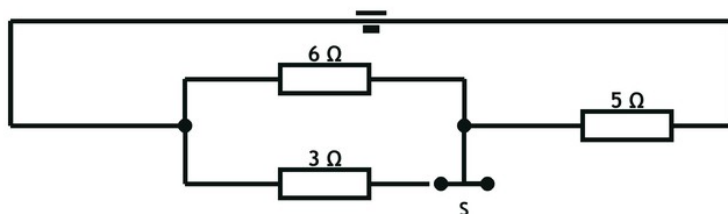

Determine the total resistance of the circuit when switch S is closed.

4

9.

A student investigates the relationship between the voltage across a lamp and the current in it, and records the following values.


Voltage (V)	0.00	0.50	1.00	1.50	2.00
Current (mA)	0	120	200	250	280

(a) On the graph paper provided, plot a graph of the results.

3

(b) Describe what happens to the resistance of the lamp as its temperature increases.

1

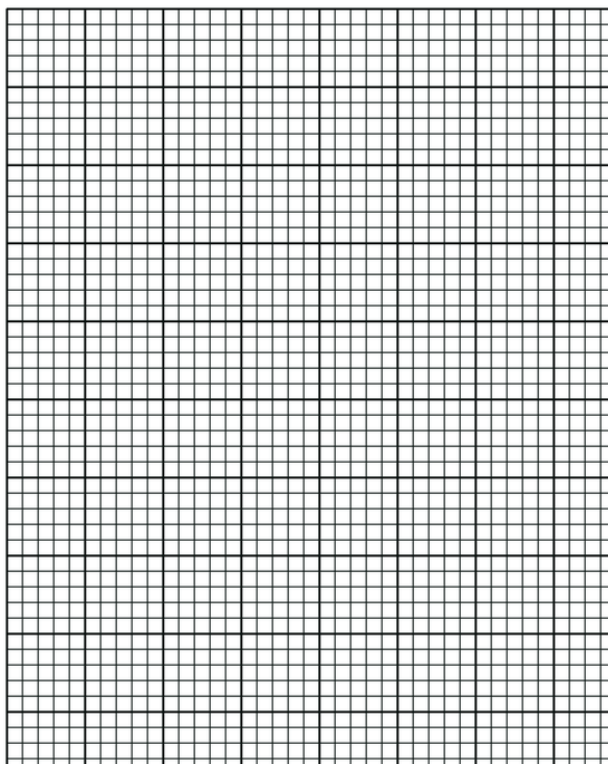

(end of question paper)

S3 Electricity 1 — Practice Test

Marking Instructions

Section A

1 B · 2 C · 3 C · 4 B · 5 C

Section B

Q6 — Resistor colour code (4)

(a) Green = 5, Blue = 6 → 56; Brown = $\times 10$ → 560 Ω 1

(b) Silver = $\pm 10\%$ 1

(c) 10% of 560 = 56 Ω ; 560 + 56 = 616 Ω 1

(d) 560 – 56 = 504 Ω 1

Accept 0.56 k Ω / 0.616 k Ω / 0.504 k Ω . (c) and (d) carry through an incorrect (a).

Q7 — Ohm's law from a circuit (3)

Converts 150 mA to 0.150 A 1

Substitutes into $R = V \div I$: $4.5 \div 0.150$ 1

$R = 30 \Omega$ (unit required) 1

A candidate who does not convert ($4.5 \div 150 = 0.03 \Omega$) scores 1 mark only.

Q8 — Combination circuit (4)

Identifies 6 Ω and 3 Ω as parallel, correct method 1

Parallel combination = 2 Ω 1

Adds the 5 Ω in series 1

Total = 7 Ω (unit required) 1

$(6 \times 3) \div (6 + 3) = 2 \Omega$; $2 + 5 = 7 \Omega$. $6 + 3 + 5 = 14 \Omega$ (treats all as series) scores 0.

Q9 — Plotting and temperature (4)

(a) Axes labelled with quantity + unit, sensible scale 1

All five points plotted accurately 1

Best-fit curve drawn (smooth, not dot-to-dot) 1

(b) Resistance increases 1

Either axis orientation accepted (V up/I across, or I up/V across) provided both axes carry quantity and unit. Accept the current axis in mA or A.

Totals: 5 + 4 + 3 + 4 + 4 = 20