


Daily Review




- 1 A microcontroller runs a stored...
- 2 One advantage in the MI's words?
- 3 An input switch goes from ... to the pin.
- 4 A motor needs what between it and a pin?
- 5 'Driver' on its own scores...

Flowcharts

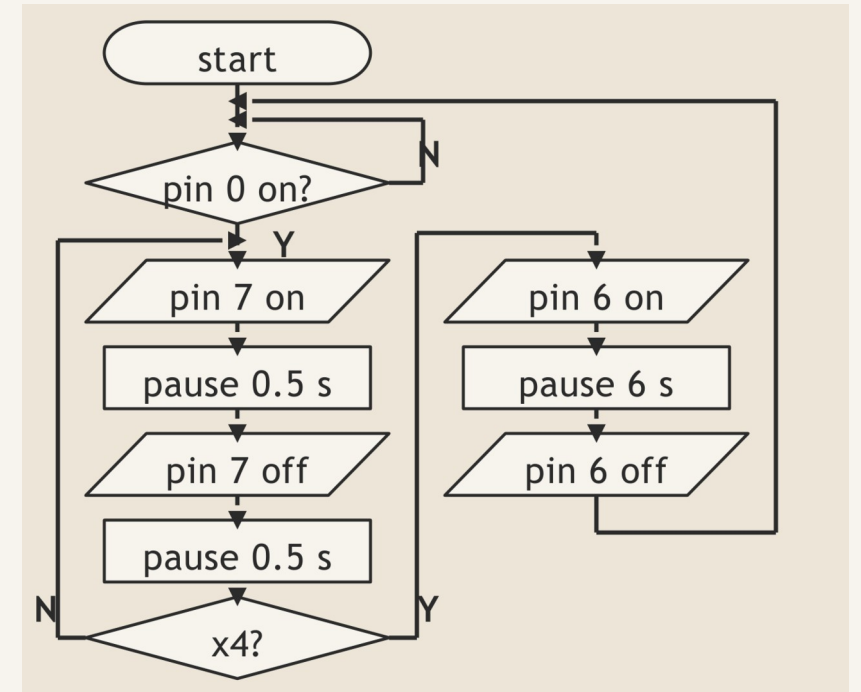How do you tell a chip what to do,
and when?



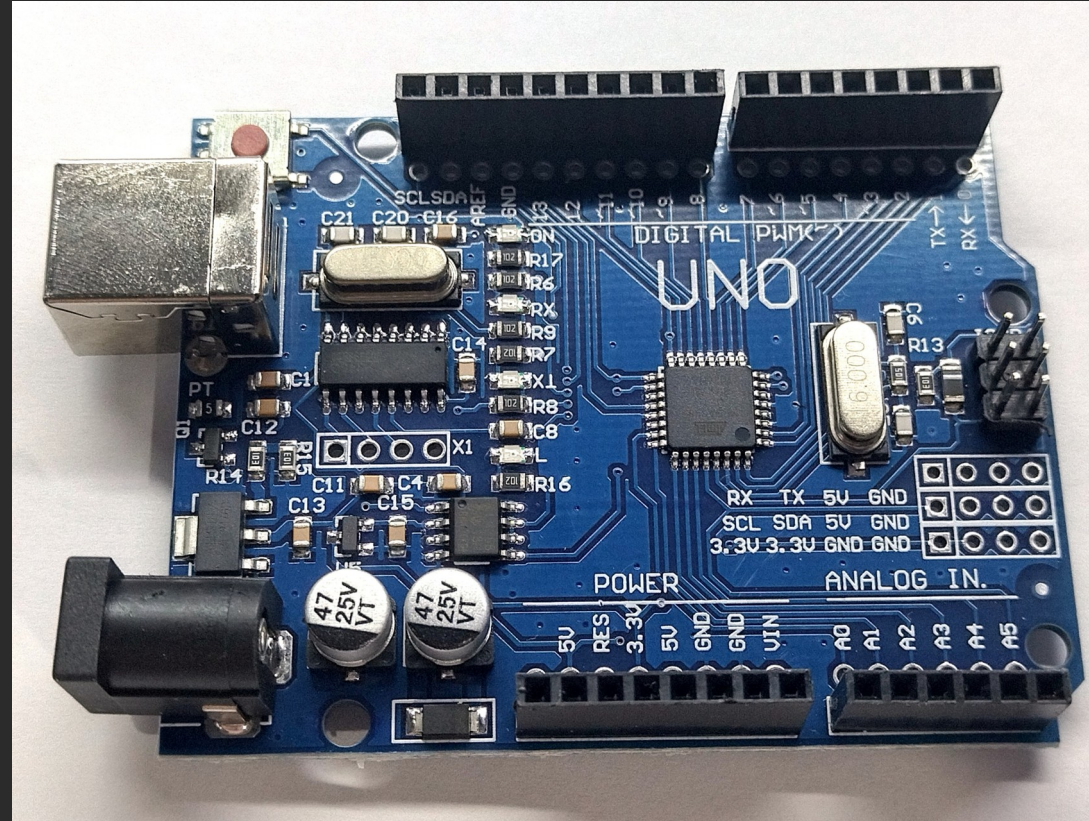How do you tell a chip: flash the lamp 3 times, then wait for the button?



The Uno we use

PART 1

Symbols and Structures

Six symbols. Four ways to put them together.

By the end of this part...



- 1 I can identify the six flowchart symbols
- 2 I can describe a continuous loop and a fixed loop
- 3 I can describe a time delay and a branch

What a Flowchart Is

A flowchart


the steps of a program, in order

Each step

one box


The lines

show the order

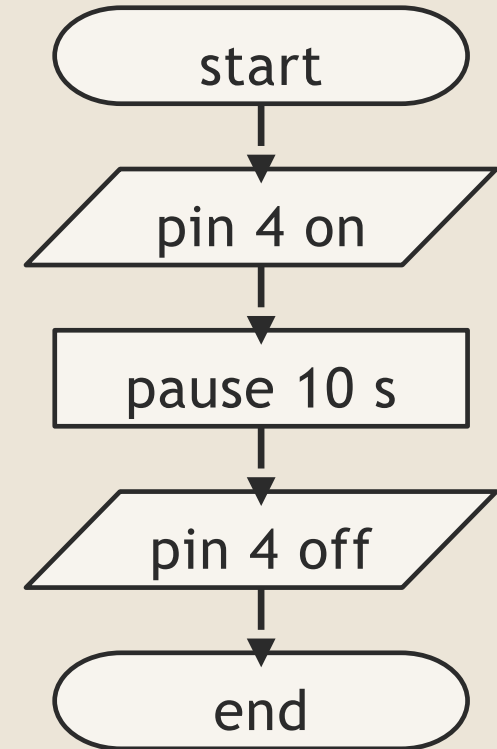

The Six Symbols

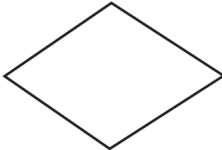

Terminator symbol		Used for the start and end of a main program or sub-procedure.
Line symbol		Shows the direction of program flow. For flow down or to the right, an arrow is not needed. For flow upwards or to the left, arrows are added.
Input/Output		Used to control outputs or to show that data is being received.
Process symbol		Used for operations which take place within the microcontroller, for example a delay.
Decision symbol		Program flow is determined by a “yes” or “no” answer to the question in the box.
Sub procedure symbol		Used to call a sub-procedure.

Lines and Arrows

Down or right


an arrow is not needed

Up or left

an arrow is needed

Every loop back

draw its arrow: the MI marks it

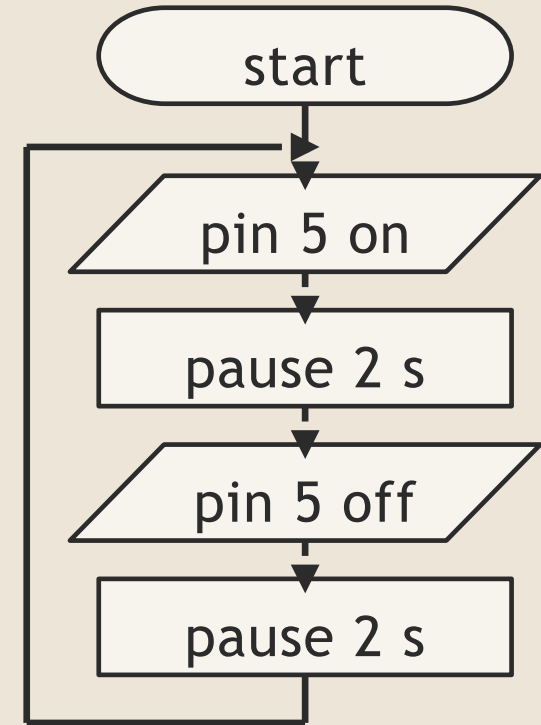

What Goes in the Box



Output

pin 7 on • pin 7 off

Input decision

pin 1 on?

Delay

pause 0.5 s (always a unit)

Fixed loop

x3?

The booklet writes

Lamp (output, pin 13) ON


Wait 1 s (1000 ms)

count < 5?


Name the Symbol




1

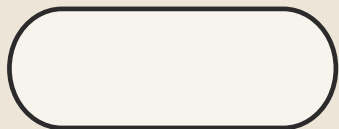


2

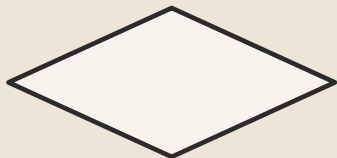


3

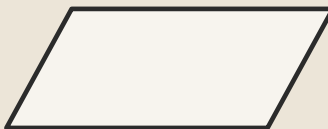

4

 

5

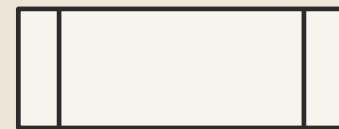

Continuous Loop




Repeats

forever, until the power goes off

Drawn as

a line back up, with an arrow

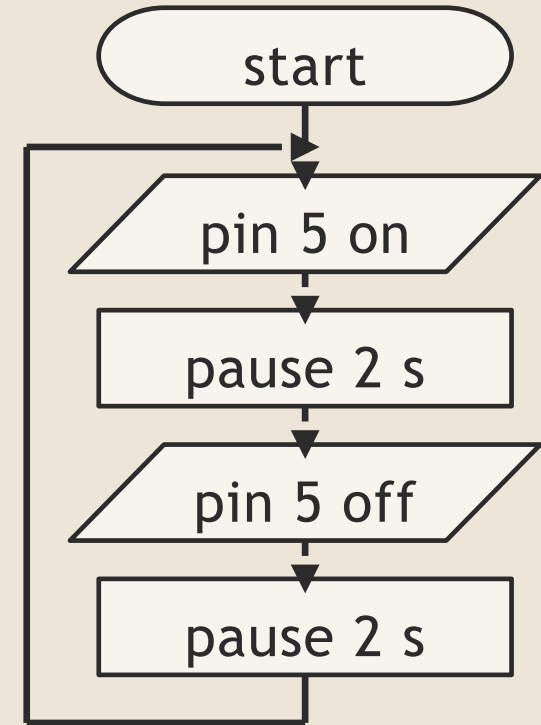

Fixed Loop




Repeats

a set number of times, then moves on

Drawn as

a decision, x3?, N loops back

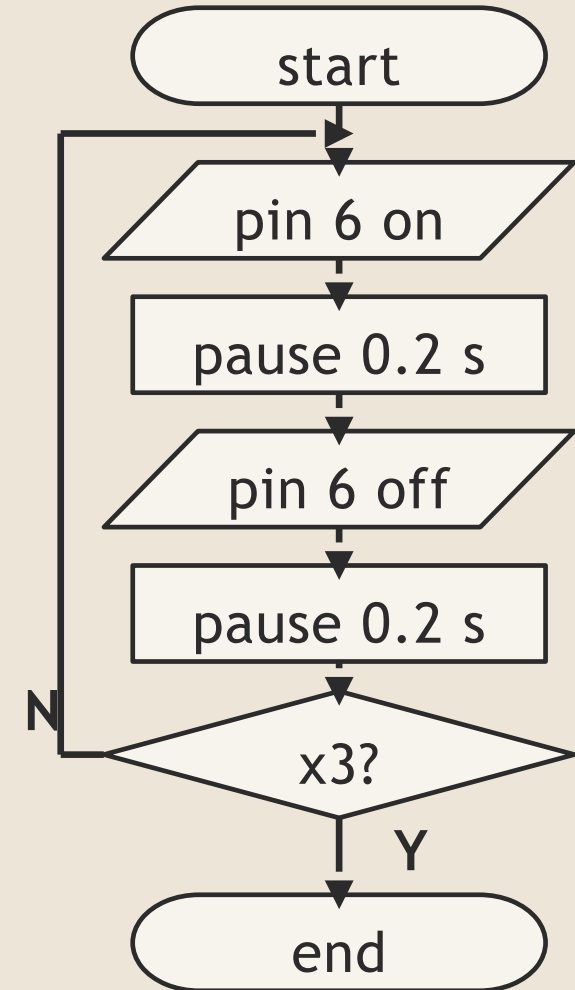

Time Delay




A pause

the program waits for a set time

Meanwhile

outputs stay as they are

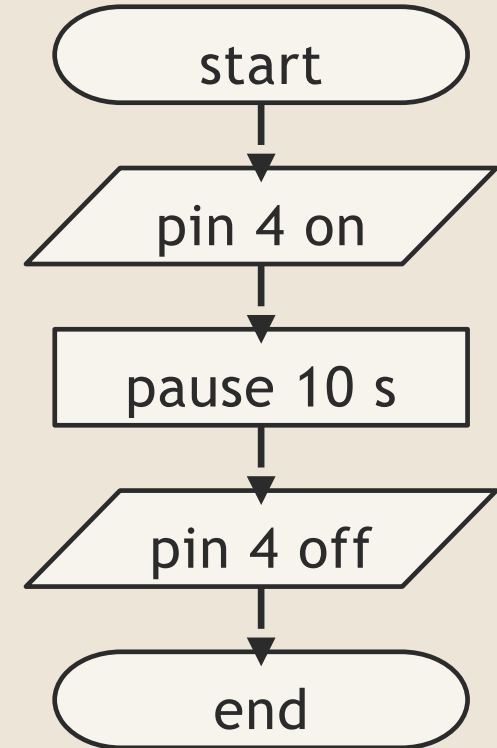

Branch




A decision

yes or no

Each answer

its own path, labelled Y and N

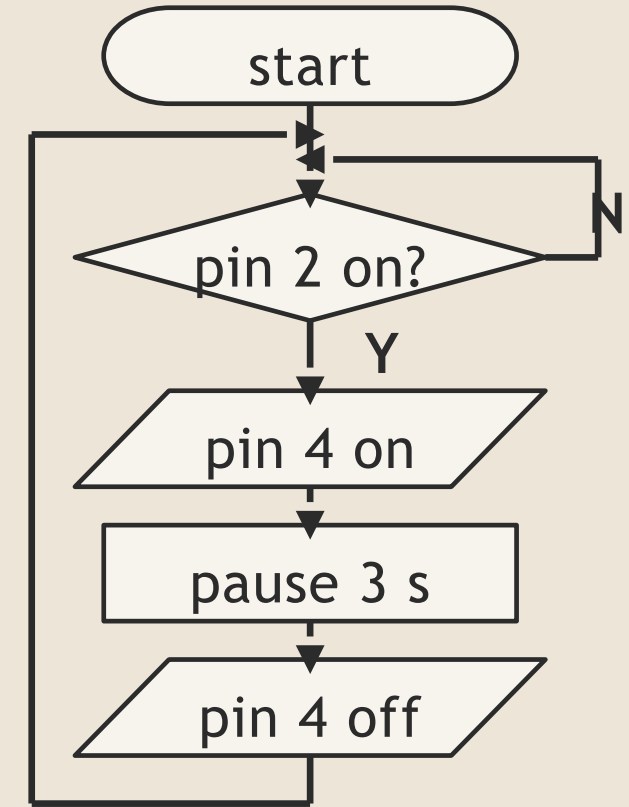

Which Structure?




- 1 A pump runs for 5 minutes, then stops.
- 2 A sign flashes all day.
- 3 A bell rings 4 times, then stops.
- 4 If the door opens, sound the alarm.
- 5 A fan waits for the switch, every time.

PRACTICE: Programming Structures



Booklet page 7

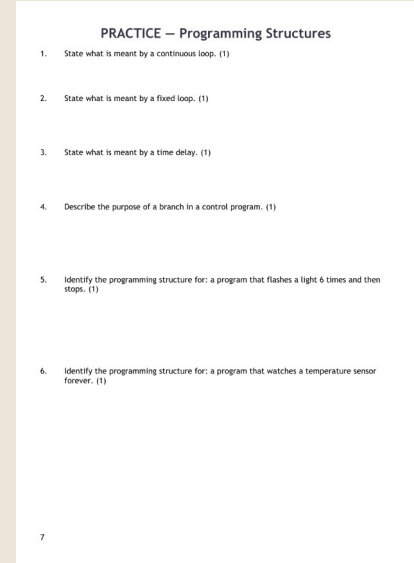Answer Q1 to Q6 on your own.
One sentence each.



6 min



Programming Structures: Answers



1 Q1 Continuous loop

2 Q2 Fixed loop

3 Q3 Time delay

Programming Structures: Answers



4 Q4 Branch

5 Q5 and Q6

Checkpoint



- 1 Which symbol holds a delay?
- 2 Which line needs an arrow?
- 3 Why does a control program loop forever?

Plenary: Part 1



- 1 The diamond is the ... symbol.
- 2 Input and output share which shape?
- 3 A loop that repeats forever is...
- 4 x3? makes what kind of loop?
- 5 During a delay, the outputs...

Look back — by the end of this part...



- 1 I can identify the six flowchart symbols
- 2 I can describe a continuous loop and a fixed loop
- 3 I can describe a time delay and a branch

Daily Review



- 1 The diamond is the ... symbol.
- 2 A delay goes in which box?
- 3 A fixed loop repeats...
- 4 Arrows are needed going...
- 5 A decision needs which two labels?

PART 2

The Exam Flowchart

10 marks, every year. Here is how they are given.

By the end of this part...



- 1 I can complete a flowchart from an I/O table
- 2 I can put every pin number and unit in
- 3 I can draw every decision with Y, N, a loop and an arrow

How the Marks Are Given



Each output: on and off, in the right place (1)

Each input decision: Y, N, a loop, an arrow (1)

Each delay: right place, with a unit (1)

x3?: Y, N, and an arrow back before the repeat (1)

A loop to the start with an arrow, or an end (1)

All the symbols right (1)

The Method



- 1 Read the I/O table: which pins are in, which are out.
- 2 Draw one box per bullet, in order, top to bottom.
- 3 Turn each input into a decision, pin 1 on?, with Y and N.
- 4 Turn each repeat into x3?, with an arrow back.
- 5 Finish: loop to start, or end. Check pins, units, arrows.

Worked Example: The Question (9 marks)



Input

train sensor: pin 0

Outputs

lamps: pin 7

barrier motor: pin 6

When the train sensor is on:

the lamps flash on and off 4 times,
0.5 s on and 0.5 s off;

the barrier motor then turns on for 6 s,
then off;

the sequence returns to the start.

Worked Example: The Answer (9 marks)



pin 0 on?: Y, N, loop (1)

pin 7 on, off (1)

Both pauses, units (1)

x4?: Y, N (1)


Arrow back (1)

pin 6 on, off (1)

pause 6 s, unit (1)

Loop to start (1)

All symbols right (1)

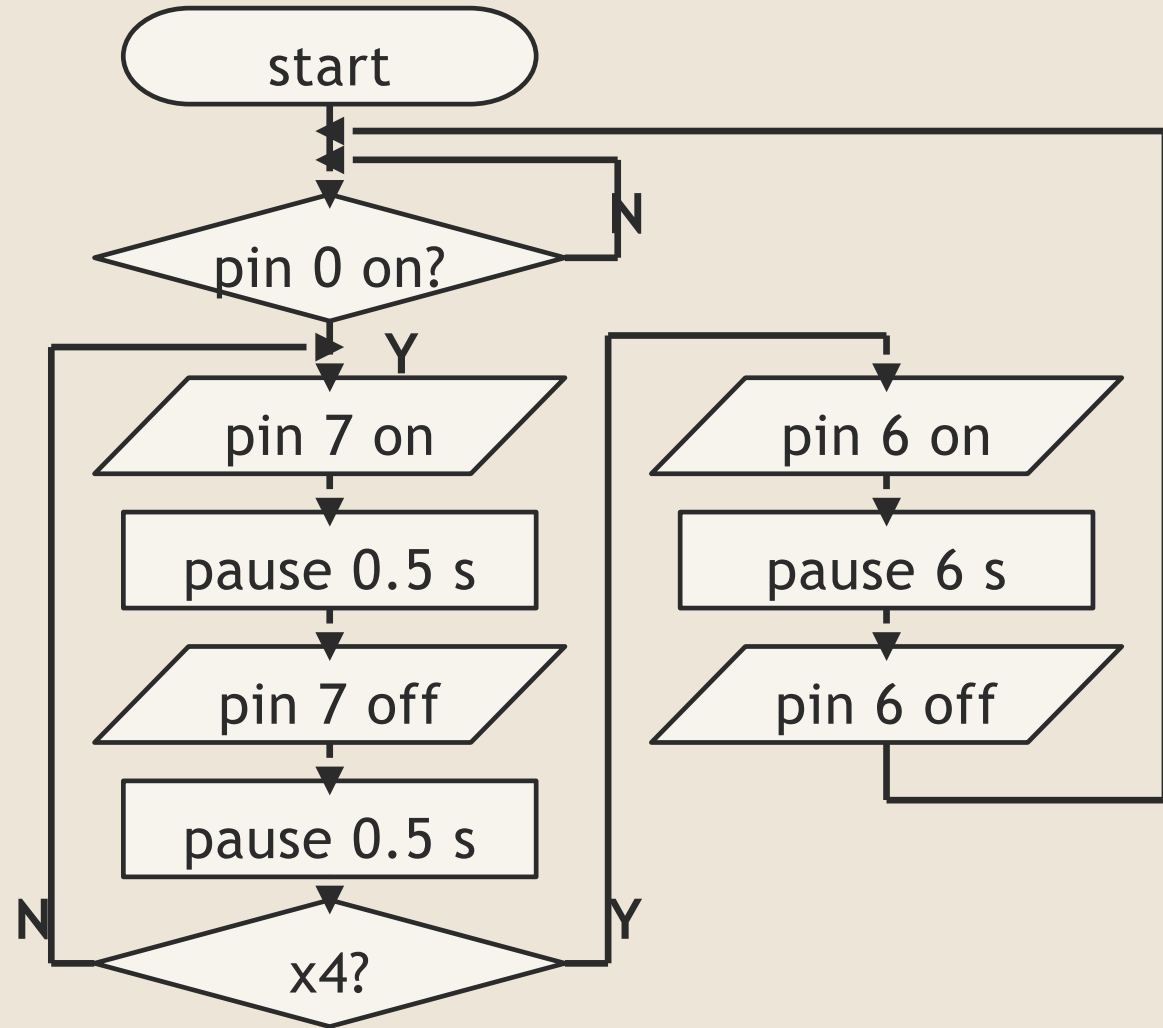

Your Turn: The Car Wash (6 marks)



Input

button: pin 1

Outputs

pump: pin 5; brush: pin 4

Pressed

pump on 20 s, off; brush on
30 s, off; repeat

start


Spot the Mistake



A pupil drew this
a lamp flashing for ever

Find
three mistakes

Each one
loses a mark

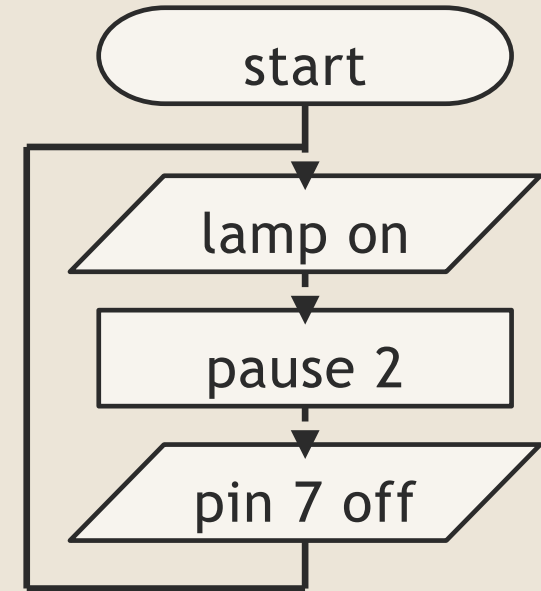


PRACTICE: Flowcharts



Booklet pages 9-13

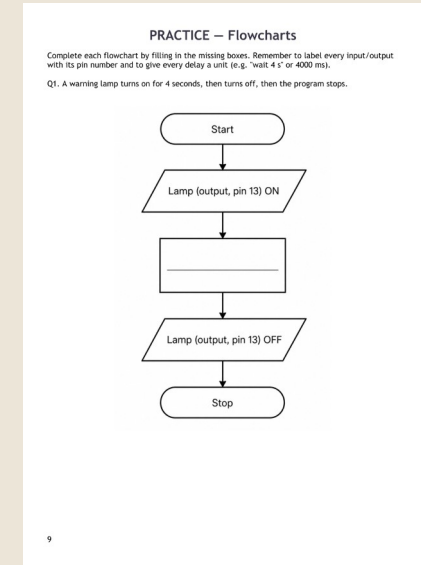Q1 to Q5: fill in the missing boxes.
Every pin number. Every unit.



12 min



Flowcharts: Answers



- 1 Q1 the blank box
- 2 Q2 the three blanks
- 3 Q3 the four blanks

Flowcharts: Answers



4 Q4 the three blanks

5 Q5 the decision

Checkpoint



- 1 What must every output box show?
- 2 What must every delay show?
- 3 Why draw the arrow on a loop back?

Plenary: Part 2



- 1 An input becomes which box?
- 2 A repeat becomes...
- 3 The N loop of x3? goes back to...
- 4 Extra boxes in the exam are...
- 5 The program ends with...

Look back — by the end of this part...



- 1 I can complete a flowchart from an I/O table
- 2 I can put every pin number and unit in
- 3 I can draw every decision with Y, N, a loop and an arrow

Daily Review



- 1 Every output box shows its...
- 2 Every delay shows its...
- 3 A loop back needs an...
- 4 x3? is what kind of loop?
- 5 Extra steps in the exam are...

PART 3

Build It, Test It

Draw it, then make it run.

By the end of this part...



- 1 I can build a flowchart in NoSyntaxSim and test it
- 2 I can build the same flowchart in Yenka
- 3 I can answer a past-paper flowchart question

NoSyntaxSim: Flowchart to Uno

Each box


picks its pin

Run Programme

lights each step

On paper

still pin 0 on?, pause 3 s

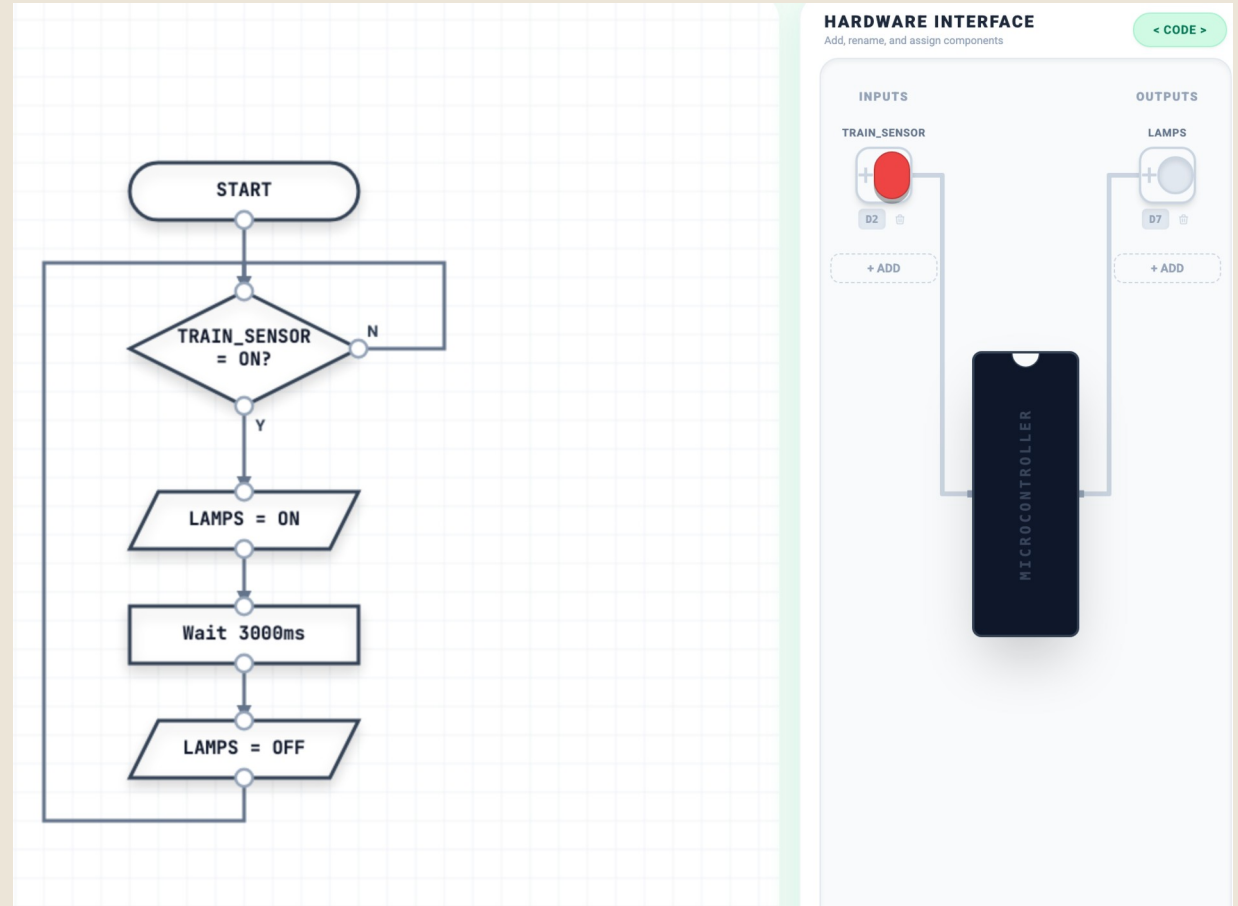

Yenka: The Same Flowchart

Same symbols

same order

Each output

set its pin

Each wait

set its time and unit

Run it

press the input, watch the output

Build It: 2022 Q9 in Both Simulators



NoSyntaxSim, then Yenka

Build the flowchart from the I/O table.
Test each input. Then build it in Yenka.

The system is operated by a microcontroller.

The input and output connections to the microcontroller are shown in the table below.

Input connections	Pin	Output connections
	7	buzzer
	6	timer
lane switch	1	
master switch	0	

The system operates using the following sequence.

- A master switch is pressed
- A buzzer then sounds on and then off three times over 1.5 seconds
- The timer then starts
- When a lane switch is pressed the timer stops
- The system will then reset ready to be used again

15 min



Past Papers: Flowcharts



The dishwasher is operated by a microcontroller.

Input and output connections to the microcontroller are shown in the table below.

Input connection	Pin	Output connection
	7	red LED
	6	water pump
	5	heating element
	4	buzzer
	3	
start switch	2	
door sensor	1	
	0	

A drying cycle used in the dishwasher operates using the following sequence:

- When a start switch is pressed a red LED will turn on.
- After a door sensor is activated a water pump will turn on for 35 seconds and then turn off.
- A heating element will then turn on for 5 minutes and then turn off.
- A buzzer will then sound six times, turning on for 0.3 seconds and turning off for 0.3 seconds each time.
- The red LED will then turn off.
- The sequence will return to the start.

2024 Q11(b) (11 marks)

In class

2022 Q9(a), 2024 Q11(b)

Homework

2021 Q13(b), 2023 Q8(a)



2022 Q9(a): 10 Marks, 1 per Line



2024 Q11(b): 11 Marks, 1 per Line



Plenary: Part 3



- 1 In NoSyntaxSim each box picks its...
- 2 Run Programme shows...
- 3 The sim writes 'Wait 3000ms'. On paper?
- 4 How do you test a decision?
- 5 Name both simulators.

Extension

EXTRA PRACTICE



- 1 Why is x3? better than 3 copies?
- 2 Where does the sub-procedure box go?
- 3 Two inputs both needed: how many decisions?

Look back — by the end of this part...



- 1 I can build a flowchart in NoSyntaxSim and test it
- 2 I can build the same flowchart in Yenka
- 3 I can answer a past-paper flowchart question

LOOKING AHEAD

Lesson 3: Reading Programs

The exam also writes it as lines of code. Can you read them?

Course Specification

Digital electronic control systems

- using correct symbols (start, stop, input, output, branch and loop) to construct flowcharts showing solutions to simple control programs, involving time delays and continuous and fixed loops

Credits (1 of 3)

The big question (The Uno we use): Photo: JrawX, CC0, via Wikimedia Commons

The Six Symbols (data booklet p.6): © Qualifications Scotland (SQA). N4/N5 Engineering Science Data Booklet, p.6, Symbols for Flowcharts.

PRACTICE: Programming Structures (booklet page): Booklet 4b pages by R Stewart.

How the Marks Are Given (marking instructions): © Qualifications Scotland (SQA). N5 Engineering Science marking instructions: 2021 Q13(b), 2022 Q9(a), 2023 Q8(a), 2024 Q11(b), 2025 Q9(a).

Worked Example: The Answer (marking-instruction layout): © Qualifications Scotland (SQA). N5 Engineering Science marking instructions: 2021 Q13(b), 2022 Q9(a), 2023 Q8(a), 2024 Q11(b), 2025 Q9(a).

Credits (2 of 3)

Spot the Mistake (marking instructions): © Qualifications Scotland (SQA). N5 Engineering Science marking instructions: 2021 Q13(b), 2022 Q9(a), 2023 Q8(a), 2024 Q11(b), 2025 Q9(a).

PRACTICE: Flowcharts (booklet page): Booklet 4b pages by R Stewart.

NoSyntaxSim: Flowchart to Uno: NoSyntaxSim V2 screenshot. Simulator by Peter Strain, NoStrainSims (sites.google.com/view/nostrainsim), free and open to all.

Build It: 2022 Q9 (question paper): © Qualifications Scotland (SQA). N5 Engineering Science 2022 Q9 and 2024 Q11, question papers and marking instructions.

Past Papers: Flowcharts (2024 Q11): © Qualifications Scotland (SQA). N5 Engineering Science 2022 Q9 and 2024 Q11, question papers and marking instructions.

Credits (3 of 3)

2022 Q9(a): 10 Marks, 1 per Line (marking instructions): © Qualifications Scotland (SQA).
N5 Engineering Science 2022 Q9 and 2024 Q11,
question papers and marking instructions.

2024 Q11(b): 11 Marks, 1 per Line (marking instructions): © Qualifications Scotland (SQA).
N5 Engineering Science 2022 Q9 and 2024 Q11,
question papers and marking instructions.

Course Specification: © Qualifications
Scotland (SQA). Course spec v2.0, p.5

R Stewart - October 2026